

**GENERAL CERTIFICATE OF EDUCATION BOARD**  
Technical and Vocational Education Examination

**JUNE 2021**

**INTERMEDIATE LEVEL**


Specialty (Specialty Code)	<b>AUTOMOBILE REPAIR MECHANICS (ARM)</b>
Subject Title	<b>ELECTRICAL AND ELECTRONIC TECHNOLOGY</b>
Subject Code No.	<b>5135</b>
Paper No.	<b>2</b>

---

**DURATION; 2Hours 30Minutes**

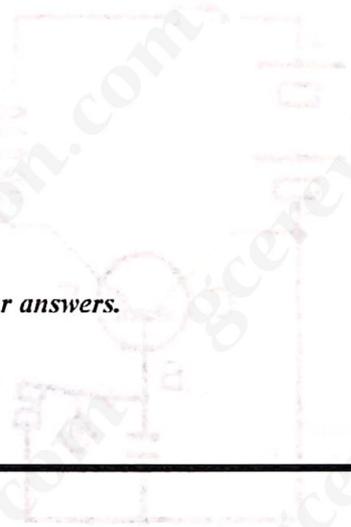**INSTRUCTIONS**

- Answer **FIVE** Questions; **THREE** from Section A and **TWO** from Section B.
- All Questions carry equal marks.
- Non-programmable calculators are allowed.
- You are reminded of the necessity for good English and orderly presentation in your answers.



---

*Turn Over*

SECTION A: TECHNOLOGY

Answer any THREE questions from this section

1. FUNDAMENTALS OF ELECTRICITY

- a) Define
  - (i) electric current (0.5mark)
  - (ii) conductor (0.5mark)
  - (iii) insulator (0.5mark)
  - (iv) semiconductor (0.5mark)
- b) Name TWO types of electric current and represent each on a v-t graph (2marks)
- c) State TWO effects of electric current and give an automobile application of each (2marks)
- d) State FOUR safety measures to be observed when working on electrical appliances (4marks)

2. IGNITION SYSTEM

The ignition system has experienced modifications since its creation. Below is a type of ignition system.

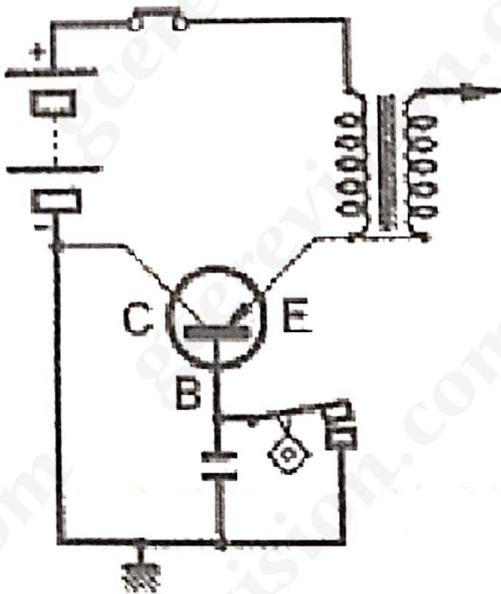


Figure 1

- a) How many key switch positions are there in general in ignition switch? Name them. (0.5+2.5marks)
- b) Identify the type of ignition system on Figure 1. (1mark)
- c) Identify the type of transistor in the circuit. (1mark)
- d) Give the function of the transistor in this system. (2marks)
- e) List THREE disadvantages of a classical coil ignition system. (3marks)

**3. FUNDAMENTALS OF ELECTRONICS**

- a) Give the function of the following electronic components
  - (i) Relay (1mark)
  - (ii) Zener diode (1mark)
  - (iii) Capacitor (1mark)
  - (iv) Transistor (1mark)
  - (v) Fuse (1mark)
- b) Define the following electronic principle terms
  - (i) Electrons (1mark)
  - (ii) Semiconductor (1mark)
  - (iii) Electromagnetism (1mark)
  - (iv) Ohms law (1mark)
  - (v) Insulator (1mark)


**4. BATTERY**

A storage battery consist of the following indications 12V75AH200A

- a) Interpret the designation
  - (i) 12V (1mark)
  - (ii) 75AH (1mark)
  - (iii) 200A (1mark)
- b) Write the chemical equation of the battery when charging and discharging. (2 marks)
- c) You receive five batteries (one 24V60AH and four 12v60AH) and a 24v75AH output battery charger.
  - (i) State FOUR test or checks to be carried out on a battery before charging. (2 marks)
  - (ii) In your answer booklet, draw a parallel circuit diagram on how you will connect the batteries during charging. (2marks)
- d) Give TWO common battery faults. (1marks)

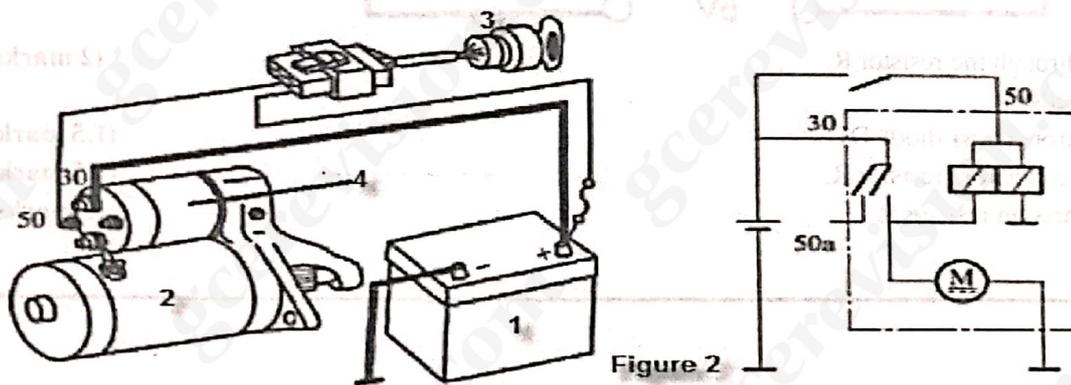**5. STARTING SYSTEM**

Automobiles are equipped with a starting system, below is a starting system circuit diagram (Figure 2)



- a) What is the function of a starting system in a vehicle? (1 mark)
- b) Identify the numbered components 1, 2, 3 and 4 of figure 2 above. (1 mark)
- c) State the function of components 1, 2, 3 and 4 of figure 2 above. (4 marks)
- d) Briefly explain in not more than six lines, the operation of the starting system (figure 2). (3 marks)
- e) Why is the starter motor mounted very close to the battery? (1 mark)

## SECTION B: PROFESSIONAL CALCULATIONS AND SCIENCE

Answer TWO questions from this section

### 6. CIRCUIT CALCULATION


- a) State the following fundamental laws of electricity
- (i) Ohms law (1mark)
  - (ii) Watts law (1mark)
- b) A 12V battery supplies three resistors  $R_1=2\text{ohms}$ ,  $R_2=5\text{ohms}$  and  $R_3=6\text{ohms}$  in parallel.
- (i) Draw a diagram to represent this circuit (1mark)
  - (ii) Calculate the total resistance of the circuit  $R_T$  (2marks)
  - (iii) Calculate the total voltage across the circuit  $V_T$  (1mark)
  - (iv) Calculate the current flowing through each resistor, hence deduce the total current (1x4marks)

### 7. CIRCUIT CIRCULATION

Figure 3 below shows a circuit containing two identical diodes.

Calculate the following when:

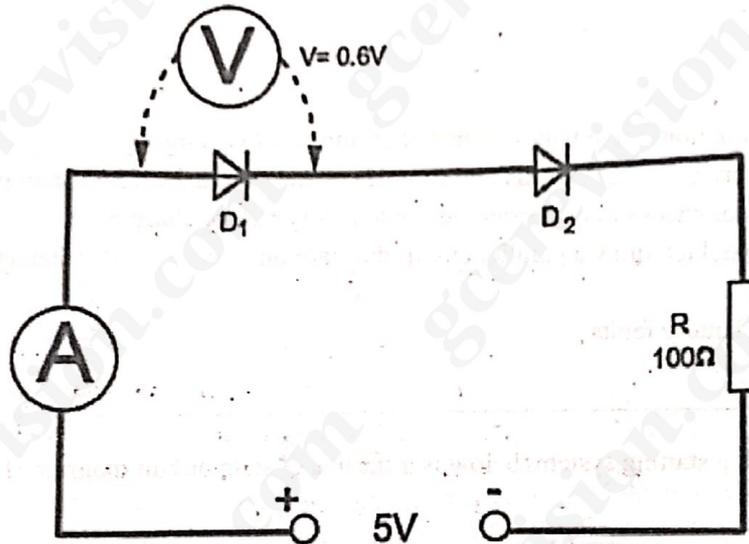- a) The circuit is serviceable (as shown)
- (i) Voltage drop across both diodes. (1.5 marks)
  - (ii) Voltage drop across the resistor R. (1.5 marks)



- (iii) Current through the resistor R. (2 marks)
- b) Diode D2 is shorted-out.
- (i) Voltage drop across diode D1. (1.5 mark)
  - (ii) Voltage drop across resistor R. (1.5 mark)
  - (iii) Current through resistor R. (2 marks)

## 8. DC MOTORS

A motor bike equipped with a direct current electric motor powered by a voltage of 18V with a power of 1800W and having a charging time of 5hours.

- a) Define the terms
- (i) Power (2 marks)
  - (ii) Efficiency (2 marks)
- b) This motor delivers a mechanical power of 1500W. Calculate its efficiency. (2 marks)
- c) Knowing that the motor has a resistance of 20ohms, determine the current absorbed, hence the power of this motor. (2+2mks)

## 9. ELECTROMAGNETISM

- a) Define the following terms
- (i) Magnetism (1 mark)
  - (ii) Electromagnetism (1 mark)
- b) Using Fleming's right hand rule, what does the thumb, forefinger and second finger each signify? (1x3marks)
- c) Give ONE effect of passing current through a straight conductor. (1 mark)
- d) The coil of a loud speaker is subjected to an electromagnetic force of value  $F=1.35\text{N}$  and a current  $I=0.25\text{A}$ .
- (i) Give TWO things that can be done to increase this electromagnetic force (0.5x2 marks)
  - (ii) Knowing that the wire of the coil has a length of 12m, calculate the magnetic field of the loud speaker (2 marks)
  - (iii) What effect does the magnet and the current have on the speaker membrane? (1 mark)